
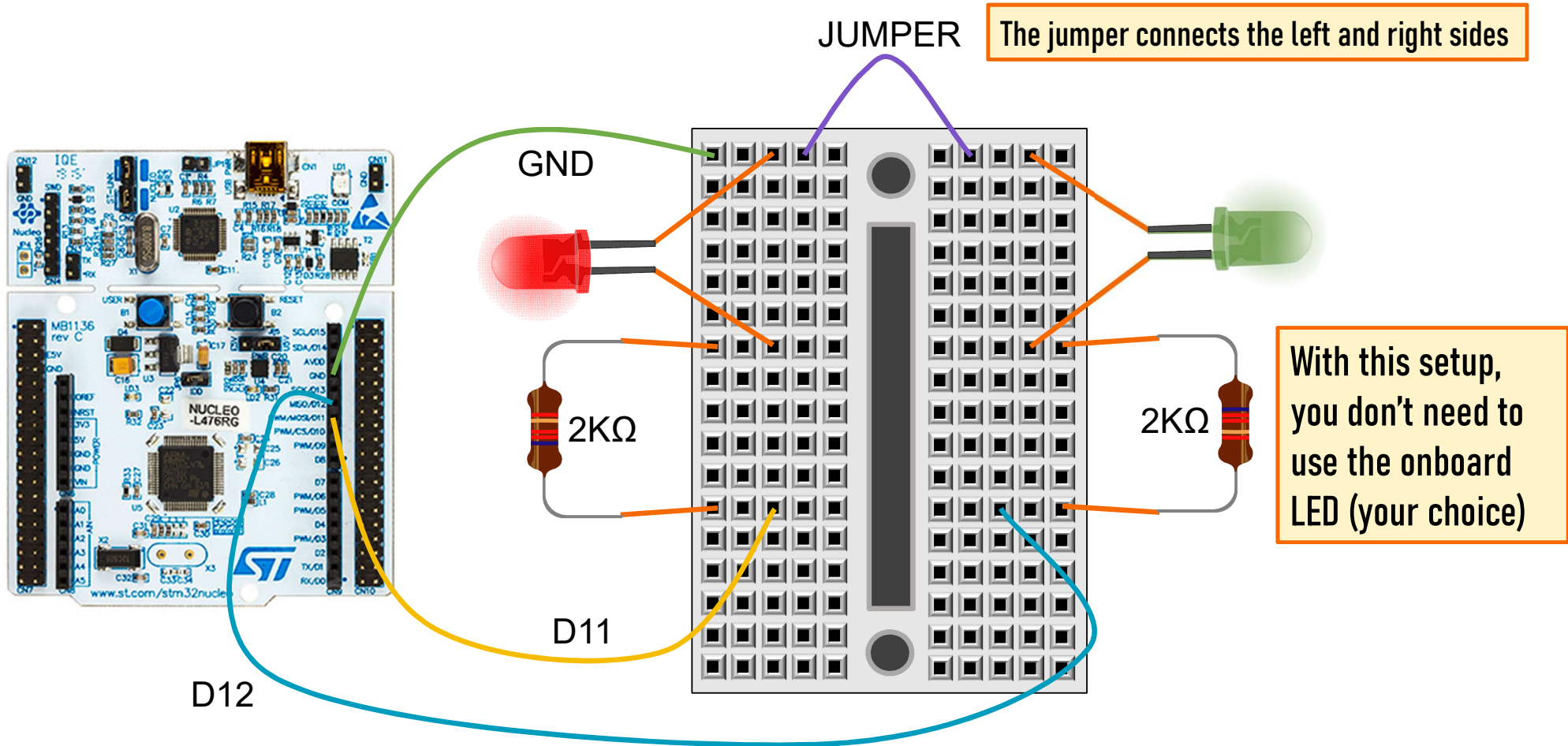


# Example LED Setup

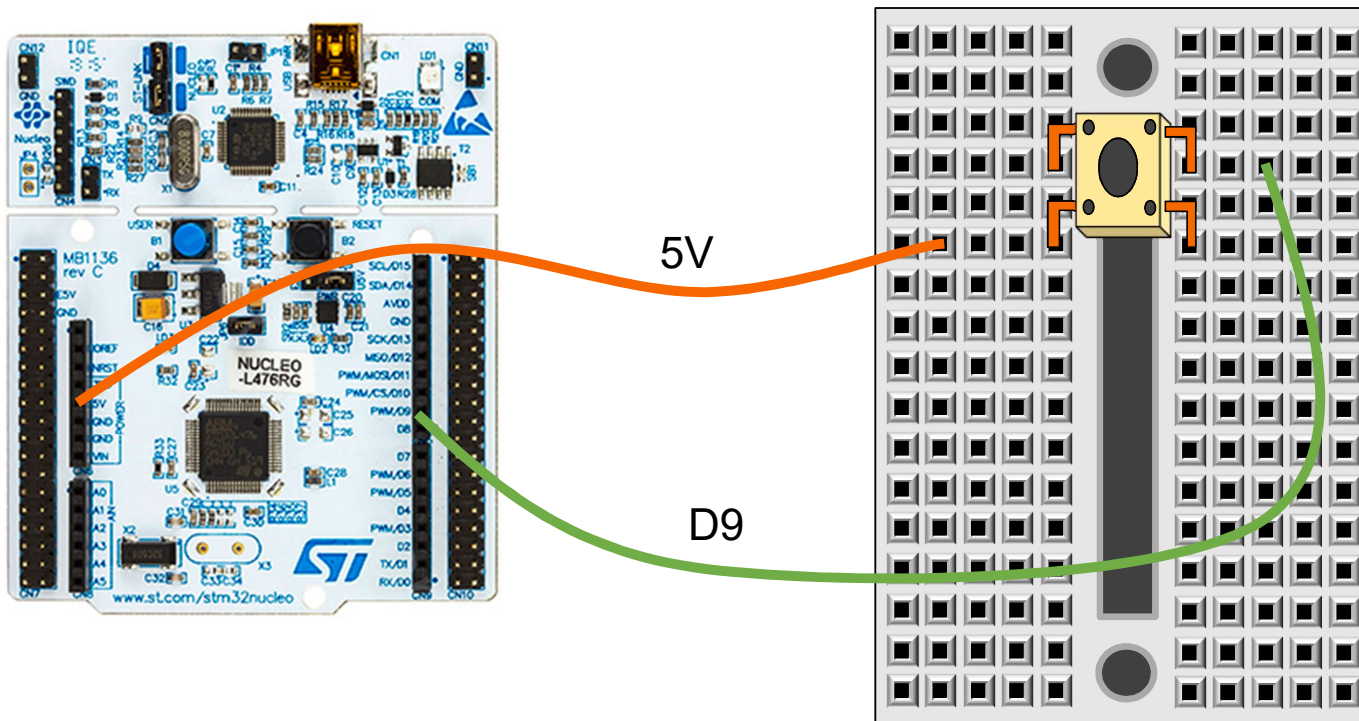

## Example Switch Setup



The switch needs to straddle the two sides of the breadboard

Wire one side to the boards 5V output and the other to a GPIO Input (D9 used here)