

Boolean Logic and Digital Circuits

Finding your Way Around

[Smart Phone / Tablet](#)

[Users See](#)

[Alternative Navigation](#)

[Below](#)

Sponsors



[Battery Performance](#)

[Improvement by](#)

[Electronic Means](#)

Modern digital computers are built from digital logic circuits whose basic building blocks are logic gates, each of which is designed to perform a specific logical function. Information is held in data "words", representing data or instructions, made up from strings of individual "bits" with their own values. These values are analogous to [Boolean logic](#) propositions and the statements or conclusions derived from them which were defined by George Boole. Boolean algebra is the tool used to design combinations of gates to implement more complex functions such as mathematical operations and data storage.

Boolean Algebra

Boolean algebra is based upon a two-valued, or binary scheme. The two values may be expressed in many ways, such as true or false, "on" or "off". It is this property which was recognised and developed by Claude [Shannon](#) in 1937 which makes it so useful for implementing digital means of electronic circuits. For example, logic 1 and logic 0 might be implemented as two different voltage levels in a circuit, or by the presence or absence of a current in the circuit.

Notation

The engineering application of Boole's logic uses a simplified version of the original notation as follows,

- **A logical OR** is equivalent to Boolean addition and is represented by a plus + sign as in $A+B \equiv A \text{ OR } B$. It can represent *parallel* switch contacts.
- **A logical AND** is equivalent to Boolean multiplication which is represented by a dot . sign as in $A.B \equiv A \text{ AND } B$. It can represent *series* switch contacts. Note that it has become conventional to drop the dot . sign (AND symbol) so that $A.B$ is written as AB .
- **A logical NOT** is equivalent to Boolean complementation or negation and is represented by an overbar $\bar{\quad}$ above the relevant letter as in \bar{A} . It can represent *normally closed* switch contacts.
- **The Exclusive OR or logical XOR** was not an original Boolean operator and has its own special symbol \oplus as in $A \oplus B \equiv \bar{A}B + A\bar{B}$. $A \oplus B$ is true but **NOT** both.

Boolean Laws

Duality

Note that every law has two expressions, (a) and (b) which are duals of each other. Duality means

- Changing every OR (+) operation of the expression to an AND (.) and every AND (.) to an OR (+).
- Changing all the 0 elements to 1's and vice-versa.

Commutative Law

(a) $A + B = B + A$

(b) $AB = BA$

Associate Law

(a) $(A + B) + C = A + (B + C)$

(b) $(AB)C = A(BC)$

Distributive Law

(a) $A(B + C) = AB + AC$

(b) $A + (BC) = (A + B)(A + C)$

Identity Laws

(a) $A + A = A$

(b) $AA = A$

(a) $AB + \bar{A}B = B$

(b) $(A+B)(\bar{A}+\bar{B}) = \bar{A}\bar{B}$

Redundance Laws

(a) $A + AB = A$

(b) $A(A + B) = A$

(a) $0 + A = A$

(b) $0A = 0$

(a) $1 + A = 1$

(b) $1A = A$

(a) $A + \bar{A} = 1$

(b) $A\bar{A} = 0$

Free Report

[Buying Batteries in China](#)

Electropaedia Pages

[Alphabetical Index](#)

[About Us](#)

[AC Batteries](#)

[AC Motors](#)

[Alkaline Batteries](#)

[Alternative Energy](#)

[Storage Methods](#)

[Apollo Moon Shot](#)

[Authentication and](#)

[Identification](#)

[Battery Applications](#)

- [Battery Comparison Chart \(PDF\)](#)
- [Battery Life \(and Death\)](#)
- [Battery Management Systems \(BMS\)](#)
- [Battery Manufacturing](#)
- [Battery Pack Design](#)
- [Battery Performance Characteristics](#)
- [Battery Power Demand Management](#)
- [Battery Protection Methods](#)
- [Battery Quotation Request](#)
- [Battery Reliability](#)
- [Battery Safety](#)
- [Battery Standards](#)
- [Battery Storage](#)
- [Battery Testing](#)
- [Battery Types](#)
- [Beginners Page](#)
- [Benefits of Custom Battery Packs](#)
- [Boolean Logic and Digital Circuits](#)
- [Brushless DC and Reluctance Motors](#)
- [Buying Batteries in China \(PDF\)](#)
- [Carbon Footprints \(Humour\)](#)
- [Cell Balancing](#)
- [Cell Chemistries](#)
- [Cell Construction](#)
- [Charger Specification Checklist](#)
- [Chargers and Charging](#)
- [Charger Quotation Request](#)
- [Common Battery Case Sizes \(PDF\)](#)
- [Communications Buses](#)
- [Communications Satellites](#)
- [Computer Architecture](#)
- [Contact Sponsors](#)
- [Contact Us](#)
- [Contacts](#)
- [Conversion Table](#)
- [DC Motors](#)
- [Direct Energy Conversion \(AMTEC\)](#)
- [Discovery of the Elements](#)
- [Electric Machines](#)
- [Electric Vehicle Charging Infrastructure](#)
- [Electrical Energy](#)
- [Electricity Demand](#)
- [Electricity from Biofuels](#)

- (a) $A + \bar{A}B = A + B$
- (b) $A(\bar{A} + B) = AB$

Involution Law

- (a) $\bar{\bar{A}} = A$

De Morgan's Theorem

- (a) $\overline{A+B} = \bar{A} \bar{B}$ (Breaking the Overbar changes the OR to an AND)
- (b) $\overline{AB} = \bar{A} + \bar{B}$ (Breaking the Overbar changes the AND to an OR)

Note: $\bar{A} \bar{B}$ is not the same as \overline{AB}

In addition to the above Boolean algebra, digital logic gates have been developed to represent Exclusive OR and Exclusive NOR e original range of Boolean laws. See [exclusive OR expressions](#) below.

Logic Gates

Logic gates may have two or more inputs and, except in some special cases, they have a single output. The status of the input and only be in one of the two binary conditions, either low (0) or high (1), represented by two different voltage levels, typically 0 volts for 5 volts for logic 1, depending on the semiconductor technology used. Logic gates also require a power supply.


The Transistor as a Switch

Electronic gates are generally constructed from transistor circuits which depend for their operation on the use of the transistor as a amplifier for which it was originally invented. With no voltage on the base, there is no current through the transistor which is thus sw (collector) voltage will be high. When a "high" voltage is applied to the base the transistor is switched on and output (collector) volta more on the page about [semiconductors](#).

An early version of a bi-stable switching circuit was the 1919 [Eccles and Jordan](#) flip-flop based on valves (vacuum tubes). The later transistor version was one of the first electronic circuits to be implemented as an Integrated Circuit by [Robert Noyce](#) in 1959.

Flip-flops rely on the concept of feedback in which the output of a circuit is fed back into the input such that when the input is high, the output is low and vice versa.

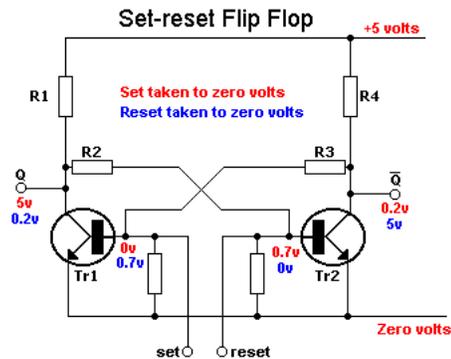See below an example of transistor switches used in the electronic circuit used to implement a [three input NOR gate](#)



Logic Gates and Truth Tables

Logic circuit truth tables show the status of the output terminal or terminals of logic gates and logic circuits for all the possible input combinations. The gate or circuit's input states are shown in the left columns of the table while the corresponding output states are shown in the right columns.

The tables opposite show the range of common logic gates with their corresponding truth tables.

Logic Gates		Truth Tables																				
<p>AND Gates</p>		<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>A.B</th> <th>$\overline{A.B}$</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	A.B	$\overline{A.B}$	0	0	0	1	0	1	0	1	1	0	0	1	1	1	1	0
A	B	A.B	$\overline{A.B}$																			
0	0	0	1																			
0	1	0	1																			
1	0	0	1																			
1	1	1	0																			
<p>OR Gates</p>		<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>A+B</th> <th>$\overline{A+B}$</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	A+B	$\overline{A+B}$	0	0	0	1	0	1	1	0	1	0	1	0	1	1	1	0
A	B	A+B	$\overline{A+B}$																			
0	0	0	1																			
0	1	1	0																			
1	0	1	0																			
1	1	1	0																			
<p>Exclusive OR Gates</p>		<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>A⊕B</th> <th>$\overline{A⊕B}$</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>1</td></tr> </tbody> </table>	A	B	A⊕B	$\overline{A⊕B}$	0	0	0	1	0	1	1	0	1	0	1	0	1	1	0	1
A	B	A⊕B	$\overline{A⊕B}$																			
0	0	0	1																			
0	1	1	0																			
1	0	1	0																			
1	1	0	1																			
<p>Inverter Negation/Inversion</p>		<table border="1"> <thead> <tr> <th>A</th> <th>\bar{A}</th> </tr> </thead> <tbody> <tr><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td></tr> </tbody> </table>	A	\bar{A}	0	1	1	0														
A	\bar{A}																					
0	1																					
1	0																					

XOR and XNOR Gates

The **Exclusive OR (XOR)** gate with inputs **A** and **B** implements the logical expression $A\oplus B = \bar{A}B + A\bar{B}$

- When both the inputs are different, then output becomes high or logic 1.
- When both the inputs are same, then output becomes low or logic 0.

- [Electricity from Fossil Fuels](#)
- [Electrochemical Energy Generation](#)
- [Electromagnetic Radiation - Radio Waves](#)
- [Electropaedia](#)
- [Technology Search Engine](#)
- [Energy Efficiency](#)
- [Energy from Coal? \(Humour\)](#)
- [Energy Resources](#)
- [Energy Conversion and Heat Engines](#)
- [Engineering Harmony. \(Humour\)](#)
- [Enigma's Cryptic Secrets](#)
- [Feedback Form](#)
- [Flow Batteries](#)
- [Free Report Request](#)
- [Frequently Asked Questions - FAQ](#)
- [Fuel Cell Comparison Chart](#)
- [Fuel Cells](#)
- [Gas Turbine Power Generators](#)
- [Generators](#)
- [Geothermal Power Generation](#)
- [Glossary](#)
- [Going Solar - Grid Scale \(PV\)](#)
- [Graphene](#)
- [Grätzel Cell](#)
- [Grid Scale Energy Storage Systems](#)
- [ESS](#)
- [Hall of Fame](#)
- [High Power Batteries](#)
- [High Temperature Batteries](#)
- [History of Technology](#)
- [Historical Themes and Characters](#)
- [Home Page](#)
- [Homebrew Battery](#)
- [How to Specify Batteries](#)
- [Hybrid Power Generation Plants](#)
- [Hydroelectric Power Generation](#)
- [Hydrogen Power](#)
- [Instructions for Using Batteries](#)
- [Lead Acid Batteries](#)
- [Leclanché Cells](#)
- [Legal Statement](#)
- [Liquid Metal Batteries](#)
- [Lithium Battery](#)
- [Shipping Regulations](#)
- [Lithium Cell Failures](#)
- [Lithium Primary Batteries](#)

The **Exclusive NOR (XNOR)** gate with inputs **A** and **B** implements the logical expression $\overline{A \oplus B} = \overline{AB + \overline{A}\overline{B}} = AB + \overline{A}\overline{B}$

- When both the inputs are same, then output becomes high or logic 1.
- When both the inputs are different, then output becomes low or logic 0.

Exclusive OR gates are commonly used for comparisons and parity checks.

The Vernam Cipher

The Vernam cipher is a special application of XOR logic. Also called **Modulo 2 Addition**, it is similar to a digital adder except that the carry digits are ignored. An important cryptography tool, its special property is that a plaintext message string can be enciphered by XORing it with a random symbol scrambler string or key of the same length to create truly unbreakable ciphertext. The ciphertext can however be deciphered directly by XORing it with the original scrambler key.

Vernam used the five bit [Baudot code](#) to represent each character with the original notation of + and - to represent the logic states, rather than the more familiar 1 and 0 used today. In the example opposite:



- The plaintext letter A is enciphered by adding a random scrambler letter, for example letter B. This generates the Baudot code for ciphertext G.
- By adding the same scrambler letter B to the ciphertext G the original plaintext letter is regenerated.

Truth Table			
Inputs		Output / Input	Output
Plaintext	Scrambler	Ciphertext	Plaintext
A	B	A⊕B = G	G⊕B=A
+	+	-	+
+	-	+	+
-	-	-	-
-	+	+	-
-	+	+	-

Three Input NOR Gate

The diagram opposite is an example of a three input NOR gate showing the electronic circuit from which the gate is constructed together with the circuit symbol for the gate and the truth table associated with the gate.

Applying a logic 1 to any of the input terminals A, B or C cause a current to flow through the load resistor R4 which in turn causes the voltage on the output terminal Z to fall to logic level 0. Only when all the input terminals are set to logic 0 will the current through the load resistor be cut off and the voltage on the output terminal will rise to logic level 1. Thus there can only be a logic 1 output if neither, A nor B nor C are set to logic 1.

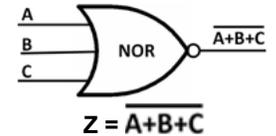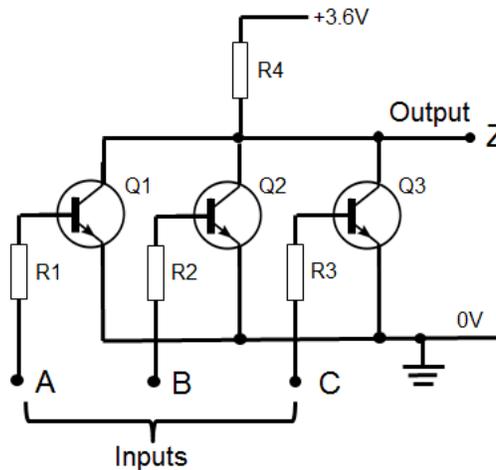

Truth Table			
A	B	C	A+B+C
0	0	0	1
0	1	0	0
0	0	1	0
0	1	1	0
1	0	0	0
1	1	0	0
1	0	1	0
1	1	1	0

Digital Logic Circuits

Boolean logic is used to design complex digital circuits to perform a wide variety of logical functions. There is however often more than one way to implement a logic circuit by using alternative types of gates. Some examples follow.

Set-Reset Flip-Flops and Latches

The Set-Reset flip-flop constructed from two cross connected, two input, NOR gates is one of the fundamental digital logic circuits. It is a bi-stable circuit which can store a single data bit in the form of a binary zero or a binary one and is used as a memory device or a latch.


Applying a logic1 to the Set terminal **S** stores a 1 and sets the output terminal **Q** to logic 1. Applying a logic 1 to the Reset terminal **R** clears the memory, storing a 0 instead and sets **Q** to logic 0. \overline{Q} is the inverse or complement of **Q**

Flip-flops or latches can also be constructed from NAND gates with similar cross connections.

Registers are common storage devices providing temporary storage of multi-bit data words such as 4, 8 or 16 bit words. They are made up of flip-flops each storing a single bit of information so that *n* flip-flops are used to store an *n* bit word.


Adders

Set-Reset Flip-Flop with NOR Gates

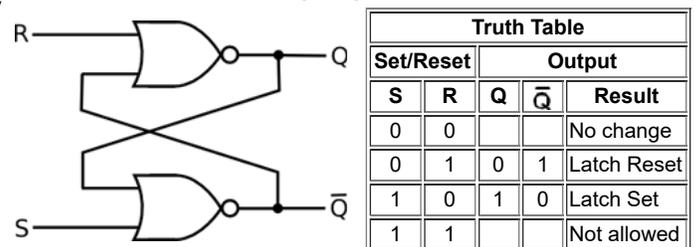


- [Lithium Secondary Batteries](#)
- [Low Power Batteries](#)
- [Magneto-Hydro-Dynamic \(MHD\) Electricity Generation](#)
- [Motor Controls](#)
- [MSDS - Typical Material Safety Data Sheet \(PDF\)](#)
- [Nickel Cadmium \(NiCad\) Batteries](#)
- [Nickel Hydrogen Batteries](#)
- [Nickel Iron \(NiFe\) Batteries](#)
- [Nickel Metal Hydride \(NiMH\) Batteries](#)
- [Nickel Zinc Batteries](#)
- [Nuclear Power - The Practice](#)
- [Nuclear Power - The Theory](#)
- [Other Galvanic Cell Chemistries](#)
- [Page Quality Rating](#)
- [Particle Physics - The Standard Model](#)
- [Piston Engine Power Generators](#)
- [Primary Batteries](#)
- [Privacy Promise](#)
- [Recycling](#)
- [Redox Batteries](#)
- [Reference Books](#)
- [Reserve Batteries](#)
- [Rocket Science](#)
- [Satellite Technologies](#)
- [Secondary Batteries](#)
- [Semiconductor Primer](#)
- [Shocking Batteries](#)
- [Silver Oxide / Silver Zinc Batteries](#)
- [Site Map **More Pages Here**](#)
- [Site Search Engine](#)
- [Small Scale Electricity Generation](#)
- [Software](#)
- [Configurable Battery](#)
- [Solar Batteries](#)
- [Solar Power Generation](#)
- [Special Purpose Motors](#)
- [Sponsors](#)
- [State of Charge \(SOC\) Determination](#)
- [State of Health \(SOH\) Determination](#)
- [Steam Turbine Power Generators](#)
- [Stirling Engine Power Generator](#)
- [Supercapacitors](#)
- [Technical Library - White Papers](#)
- [Thermal Batteries](#)

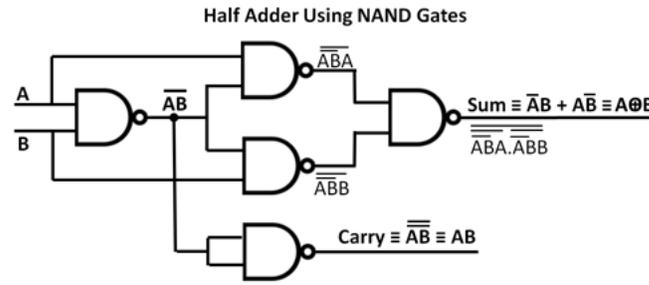The circuit opposite is a single bit half adder built from five NAND gates. Half adders have only two inputs for the two bits to be added and can not accept a carry bit from a previous stage. They do however have two outputs, one for the Sum and the other for the Carry output from the two bit addition.




Truth Table			
A	B	Sum	Carry
0	0	0	0
1	0	1	0
0	1	1	0
1	1	0	1

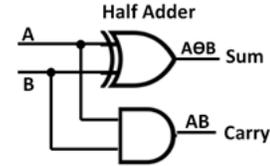The half adder opposite is another example of how logic functions can be implemented in different ways. In this case the adder circuit can be simplified by using only two gates, an AND gate and an XOR gate to perform the same half adder function as the circuit above.



Full adders are designed to accept a carry bit from a previous stage and hence have three inputs. The circuit below is an example constructed entirely from two input NOR gates. In this case it is essentially two, two-input, half adders in series with the input carry and being added to the sum of the two input bits from the first adder, in the second adder.

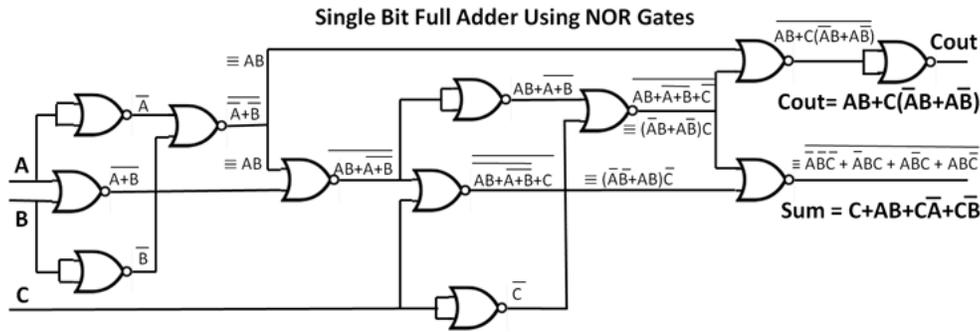Note that it takes 12 such gates simply to add two single bits plus any input carry bit from a previous addition stage and to provide the sum of the bits and any associated carry bit. A logic circuit designed to add two eight bit words will require eight times



Truth Table				
Inputs			Outputs	
A	B	C _{in}	Sum	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

It may seem strange to use so many gates when the circuit could easily be implemented with fewer, more complex gates, but circuit above were used in the **Apollo Guidance Computer** which took the US astronauts to the Moon in 1969. All of its digital circuits were **NOR gates**. This was because they needed highly reliable semiconductor components and at the time (1966) when the computer's integrated circuit technology was still in its infancy and NASA wanted to limit the number of different components used to those with record. NOR gates were chosen because they were one of the very few options that met this requirement and because NOR gates were versatile than other available gates for building more complex functions.

Binary Arithmetic

A binary adder can be adapted to perform other arithmetic operations such as subtract, multiply and divide as well as other more complex functions, avoiding the need for multiple specialist processors, by making use of the following principles of binary arithmetic.

- A 1's complement of a number is the same as the number with all its 1's changed to 0's and all its 0's changed to 1's. This is used by the adder to deal with negative numbers and subtraction.
- A 2's complement is the same as a 1's complement with the addition of an extra 1 to the least significant bit.
- The sign of a positive or negative binary number is changed by taking its 2's complement.
- A left shift of all the bits in a binary number by 1 position is the same as multiplying the number by 2 (binary 10).
- A right shift of all the bits by 1 position is the same as dividing the number by 2 (binary 10).
- A number can be raised by the *n*th power of 2 by adding *n* zeros to the end of the number.
- Multiplying a multi-bit number by 1 results in the same number. Multiplying it by 0 results in 0 and can be ignored. This multiplication is very simple.
- Dividing a multi-bit number by 1 returns the same number.
- Dividing any number by 0 is not permitted.
- Multiplication of two multi-bit numbers involves repeating the "left shift and multiply" operations *n* times in a loop, where *n* is the number of bits in the multiplier.
- Division of two multi-bit numbers involves repeating the "right shift and divide" operations *m-n* times in a loop, where *m* is the number of bits in the dividend (the number being divided) and *n* is the number of bits in the divisor.
- Subroutines carry out a series of instructions to perform arithmetic operations.

The following are three of the most common examples.

- **Subtraction**

To subtract binary number B (the subtrahend) from binary number A (the minuend).

- Add the 2's complement of B to A
- If there is a final carry bit, discard it and the result is positive.
- If B greater than A there will be no carry bit and the result will be the 2's complement of the sum and is negative.
- (There's a slightly different way of making the subtraction with the 1's complement of B instead of the 2's complement)

- **Base**
The reference number on which the exponent is based.
- **Exponent**
It is the power to which the base is raised.
It indicates where the decimal (or binary) point is placed relative to the beginning of the significand.
- **Radix**
The binary equivalent to the decimal point in decimal numbers.

Example

In scientific notation the decimal number 345.6 can be represented by 3.456×10^2 where 3456 is the mantissa or significand, 10 is exponent.

Floating Point Number Benefits

- They can represent numbers of widely different magnitudes (Range is limited by the length of the exponent)
- They provide the same relative accuracy at all magnitudes (Accuracy is limited by the length of the significand)
- In calculations involving numbers with both very large and very small magnitudes they enable the accuracy of both to be p

Floating Point (FP) Operations

Floating point operations can be implemented by hardware (circuitry) or by software (program code). Software is however much slower two or three orders of magnitude.

Bit Shifting

Shifting the mantissa left by 1 bit decreases the exponent by 1 and moves the radix point right by one place.
Shifting the mantissa right by 1 bit increases the exponent by 1 and moves the radix left by one place.

Basic FP Algebraic Functions

- **FP Addition**
 - Align the decimal points by increasing or decreasing one of the exponents so that both exponents are the same. mantissa for the sum.
 - Change the corresponding mantissa accordingly.
 - Add the new mantissas to get a new mantissa for the sum.
- **FP Subtraction**
 - Align decimal points and change the mantissa as above
 - Subtract using 2's complement
- **FP Multiplication**
 - Multiply the mantissas to get the new mantissa
 - Add the exponents to get the new exponent
- **FP Division**
 - Divide the mantissas to get the new mantissa
 - Subtract the exponents to get the new exponent

Transcendental and Other Functions

It is possible, but not necessarily practical, to store all the required values of transcendental functions in look-up tables stored in the memory. While this would be convenient, in many applications however, it would require impractically large memories. Instead the necessary values are calculated as required.

Estimating the value of a transcendental function involves setting up a loop to calculate the value of each significant term in the series and store the values in a separate accumulator (taking the sign into account). The more the terms in the series, the better will be the accuracy. The time will be correspondingly longer due to the increased number of calculations.

It is often possible to represent the transcendental function using alternative mathematical approximation methods. As in the trade-off between accuracy above, the alternative methods also involve similar trade-offs. The Taylor series is a common mathematical expansion, that is used to approximate the value of transcendental functions. Some typical examples using the Taylor series follow.

See more about the [Taylor series](#).

See also the [CORDIC](#) expansion (below).

- **Trigonometric Functions**

- The following series are the Taylor expansions for the sine and cosine where the variable X is measured in radians

$$\sin(X) \approx X - \frac{X^3}{3!} + \frac{X^5}{5!} - \frac{X^7}{7!} + \dots + (-1)^i \frac{X^{(2i+1)}}{(2i+1)!} + \dots$$

$$\cos(X) \approx 1 - \frac{X^2}{2!} + \frac{X^4}{4!} - \frac{X^6}{6!} + \dots + (-1)^i \frac{X^{(2i)}}{(2i)!} + \dots$$

Note that these two series involve both positive and negative terms and the denominators involve increasing factorials. The terms will converge very quickly to small magnitudes.

Note also that the computer does not usually calculate the numerical values of the factorials which are instead read from tables in the memory.

An alternative to the Taylor series for estimating the value of the sine function is the [Hastings approximation](#) which is faster and only slightly less accurate.

The function is divided into a small number of intervals and, in each of these, a straight line approximation is used. The straight line segments have denominators which are powers of 2, and so the calculation does not need floating point

division operations. This was the algorithm used for trigonometric calculations in the Apollo 11 Guidance Computer astronauts to the Moon.

- **Logarithms**

- The following is the Taylor expansion for the natural logarithm (**ln**).

$$\ln(Z) \approx \frac{(Z-1)^1}{1} - \frac{(Z-1)^2}{2} + \frac{(Z-1)^3}{3} - \frac{(Z-1)^4}{4} + \dots + (-1)^i \frac{(Z-1)^i}{(i)} + \dots$$

This is valid for any real number Z that satisfies $0 < Z < 2$.

- **Exponential**

- This is the Taylor expansion for the exponential (e^Z)

$$\exp(Z) \approx 1 + Z + \frac{Z^2}{2!} + \frac{Z^3}{3!} + \frac{Z^4}{4!} + \frac{Z^5}{5!} + \dots + \frac{Z^i}{(i)!} + \dots$$

Note that all the terms in this series are positive and the numerators increase more quickly than the denominator not converge but expands.

- **Square Root**

The square root is not a transcendental function. Numerous ways for calculating square roots have been developed since was proposed by the Greek mathematician [Hero of Alexandria](#) in the first century A.D.

- **Iterative Method**

The simple method based on "guess, check and refine" has been used for many years. It works as follows where root \sqrt{x}

1. Guess an answer "a" between 0 and x.
2. Calculate a^2
3. Find the error E in the answer $E = x - a^2$
4. If E is a positive number, a is too small.
If E is a negative number, a is too big.
5. If the magnitude of E is sufficiently small, $a = \sqrt{x}$
6. If the error E is too big modify a, return to step 2 and repeat.

The magnitude of E will progressively decrease until the desired accuracy is reached.

This method was designed for use with decimal numbers. It is not so convenient with binary numbers and can lead to a large number of loops to converge on an acceptable answer. Extra steps in this simple program can improve this.

- **Direct Method**

The square root can be calculated directly by using the properties of natural or base 10 logarithms but the logarithmic transcendental functions and the values must first be extracted from a suitable approximation routine such as the method depends on the following properties of the natural logarithm (**ln**):

- $\ln X^n = n \ln X$
and
- $e^{\ln X} = X$

The answer is given by: $\sqrt{x} = e^{(\ln X)/2}$ using the natural logarithm (**ln**)

Alternatively, using the base 10 logarithm (**log**), the answer is given by: $\sqrt{x} = 10^{(\log X)/2}$

(Dividing the exponent by 2 generates a square root, the same as with logarithmic tables).

Pocket calculators typically use this method of calculating square roots.

CORDIC Approximation Algorithms

The CORDIC algorithm is an iterative method for calculating transcendental functions using only binary *shift* and *add* operations.

Using the example of calculating the value of a tangent, $X/Y = \tan \Theta$, expressed in the form $\tan(2^{-n})$

A vector from the origin (zero) is rotated in a series of "n" small steps $\delta\Theta$ so that the sum of all the steps is equal to Θ . By accumulating changes in the values of its orthogonal coordinates δX and δY at each step, the values of X and Y and hence the tangent can be calculated. Described by J.E. [Volder](#) in 1959, the CORDIC algorithm was used in the first scientific hand-held calculator (the HP-35) and various other concepts have since been developed and refined for approximating a wide variety of transcendental functions.

 [Print This Page](#) || [Home](#) || [FAQ](#) || [Site Map](#) || [Legal](#) || [Privacy Promise](#) || [Contacts](#)

Woodbank Communications Ltd, South Crescent Road, Chester, CH4 7AU, (United Kingdom)
Copyright © Woodbank Communications Ltd 2005